

Circuit A POS MAXTERMS

AB	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$$(C+0) \cdot (\bar{C}+0) \cdot (\bar{A})$$

$$D \cdot \bar{A}$$

Equation $\rightarrow$ circuit - a.v

Circuit B SOP MINITERMS

AB	00	01	11	10
00	1	1	1	1
01			1	
11			1	
10		1	1	

$$(\bar{C}\bar{D}) + (\bar{D}B) + (AB)$$

Equation $\rightarrow$ circuit - b.v